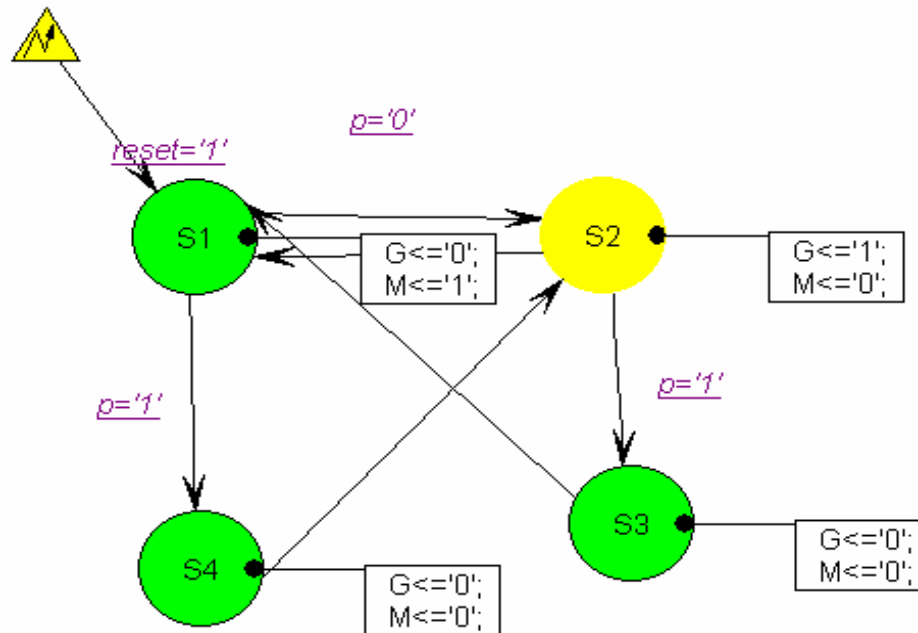
 
 
 


Esempio FSM

Entity: esempioFSM
Architecture: esempioFSM_arch



```

-----
--
-- Description :
--
-----

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity esempioFSM is
    port (
        clk: in STD_LOGIC;
        p: in STD_LOGIC;
        reset: in STD_LOGIC;
        G: out STD_LOGIC;
        M: out STD_LOGIC);
end;

architecture esempioFSM_arch of esempioFSM is

    -- SYMBOLIC ENCODED state machine: Sreg0
    type Sreg0_type is (S1, S2, S3, S4);
    -- attribute enum_encoding of Sreg0_type: type is ... -- enum_encoding attribute is

    signal Sreg0: Sreg0_type;

begin
    -- concurrent signals assignments
    -- diagram ACTION

    -----
    -- Machine: Sreg0
    -----

    Sreg0_machine: process (clk, reset)
    begin
        if reset='1' then
            Sreg0 <= S1;
            -- Set default values for registered outputs/signals and for variables
            -- ...
        elsif clk'event and clk = '1' then
            -- Set default values for registered outputs/signals and for variables
            -- ...
            case Sreg0 is
                when S1 =>
                    if p='1' then
                        Sreg0 <= S4;
                    elsif p='0' then
                        Sreg0 <= S2;
                    end if;
                when S2 =>
                    if p='1' then
                        Sreg0 <= S3;
                    elsif p='0' then
                        Sreg0 <= S1;
                    end if;
                when S3 =>
                    Sreg0 <= S1;
                when S4 =>
                    Sreg0 <= S2;
                when others =>
                    null;
            end case;
        end if;
    end process;
end;

```

```
end process;

-- signal assignment statements for combinatorial outputs
G_assignment:
G <= '0' when (Sreg0 = S1) else
      '1' when (Sreg0 = S2) else
      '0' when (Sreg0 = S3) else
      '0' when (Sreg0 = S4) else
      '0';

M_assignment:
M <= '1' when (Sreg0 = S1) else
      '0' when (Sreg0 = S2) else
      '0' when (Sreg0 = S3) else
      '0' when (Sreg0 = S4) else
      '1';

end esempioFSM_arch;
```

-- An odd parity checker as an FSM using VHDL.
-- Coding style: One process Mealy.

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY fsm IS
  PORT( clk, reset: IN std_logic;
        x: IN std_logic;
        y: OUT std_logic);
END ENTITY fsm;

ARCHITECTURE mealy_2p OF fsm IS
  TYPE state_type IS (even, odd);
  SIGNAL current_state: state_type;
  SIGNAL next_state: state_type;
BEGIN
  cs: PROCESS (clk, reset)
  BEGIN
    IF reset = '1' THEN
      current_state <= even;
    ELSIF rising_edge (clk) THEN
      current_state <= next_state;
    END IF;
  END PROCESS cs;
  ns: PROCESS (current_state, x) BEGIN
    CASE current_state IS
      WHEN even =>
        IF x = '1' THEN
          y <= '1';
          next_state <= odd;
        ELSE
          y <= '0';
          next_state <= even;
        END IF;
      WHEN odd =>
        IF x = '1' THEN
          y <= '0';
          next_state <= even;
        ELSE
          y <= '1';
          next_state <= odd;
        END IF;
    END CASE;
  END PROCESS ns;
END ARCHITECTURE mealy_2p;
```

-- An odd parity checker as an FSM using VHDL.
-- Sample textbench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY fsm_tb IS
END ENTITY fsm_tb;
ARCHITECTURE tb_arch OF fsm_tb IS
  COMPONENT fsm
    PORT(
      clk, reset: IN std_logic;
      x: IN std_logic;
      y: OUT std_logic);
  END COMPONENT fsm;
  SIGNAL clk, reset, x, y: std_logic;
  FOR fsm_mealy_2p: fsm USE ENTITY work.fsm(mealy_2p);
BEGIN
  clock: PROCESS IS
  BEGIN
    clk <= '0';
    WAIT FOR 20 ns;
    clk <= '1';
    WAIT FOR 20 ns;
  END PROCESS clock;

  sg: PROCESS IS
  BEGIN
    reset <= '1';
    WAIT FOR 10 ns;
    reset <= '0';
    x <= '0';
    WAIT FOR 10 ns;
    ASSERT y = '0'
      REPORT "Error: state even when x = 0"
      SEVERITY warning;
    WAIT FOR 10 ns;
    x <= '1';
    WAIT FOR 10 ns;
    ASSERT y = '1'
      REPORT "Error: state even when x = 1"
      SEVERITY warning;
    WAIT FOR 10 ns;
    x <= '0';
    WAIT FOR 10 ns;
    ASSERT y = '1'
      REPORT "Error: state odd when x = 0"
      SEVERITY warning;
    WAIT FOR 10 ns;
    x <= '1';
    WAIT FOR 10 ns;
    ASSERT y = '0'
      REPORT "Error: state odd when x = 1"
      SEVERITY warning;
    WAIT;
  END PROCESS sg;

  fsm_mealy_2p: fsm PORT MAP (clk, reset, x, y);
END ARCHITECTURE tb_arch;
```

```

1  -----
2  --      Package name: STD_LOGIC_ARITH
3  --
4  --      Purpose:
5  --          A set of arithmetic, conversion, and comparison functions
6  --          for SIGNED, UNSIGNED, SMALL_INT, INTEGER,
7  --          STD_ULOGIC, STD_LOGIC, and STD_LOGIC_VECTOR.
8  -----
9
10 library IEEE;
11 use IEEE.std_logic_1164.all;
12
13 package std_logic_arith is
14
15     type UNSIGNED is array (NATURAL range <>) of STD_LOGIC;
16     type SIGNED is array (NATURAL range <>) of STD_LOGIC;
17     subtype SMALL_INT is INTEGER range 0 to 1;
18
19     -----
20     -- add operators
21     -----
22     function "+" (L: UNSIGNED; R: UNSIGNED) return UNSIGNED;
23
24     function "+" (L: SIGNED; R: SIGNED) return SIGNED;
25
26     [...]
27
28     function "+" (L: UNSIGNED; R: UNSIGNED) return
29 STD_LOGIC_VECTOR;
30
31     function "+" (L: SIGNED; R: SIGNED) return STD_LOGIC_VECTOR;
32
33     [...]
34     -- subtract operators
35     -----
36     function "-" (L: UNSIGNED; R: UNSIGNED) return UNSIGNED;
37
38     [...]
39
40     -----
41     -- unary operators
42     -----
43     function "+" (L: UNSIGNED) return UNSIGNED;
44
45     function "+" (L: SIGNED) return SIGNED;
46
47     function "-" (L: SIGNED) return SIGNED;
48
49     [...]
50
51     -----
52     -- multiplication operators

```

```

53      -----
54      function "*" (L: UNSIGNED; R: UNSIGNED) return UNSIGNED;
55
56      -----
57      -- less_than comparison
58      -----
59      function "<" (L: UNSIGNED; R: UNSIGNED) return BOOLEAN;
60
61      -----
62      -- conversion operators
63      -----
64      function CONV_INTEGER(ARG: INTEGER) return INTEGER;
65
66      function CONV_INTEGER(ARG: UNSIGNED) return INTEGER;
67
68      function CONV_INTEGER(ARG: SIGNED) return INTEGER;
69
70      [...]
71
72      function CONV_UNSIGNED(ARG: INTEGER; SIZE: INTEGER) return
UNSIGNED;
73      [...]
74
75      function CONV_STD_LOGIC_VECTOR(ARG: INTEGER; SIZE: INTEGER)
return STD_LOGIC_VECTOR;
76
77      function CONV_STD_LOGIC_VECTOR(ARG: UNSIGNED; SIZE: INTEGER)
return STD_LOGIC_VECTOR;
78
79      function CONV_STD_LOGIC_VECTOR(ARG: SIGNED; SIZE: INTEGER)
return STD_LOGIC_VECTOR;
80
81      function CONV_STD_LOGIC_VECTOR(ARG: STD_ULOGIC; SIZE: INTEGER
) return STD_LOGIC_VECTOR;
82
83      end Std_logic_arith;
84
85
86
87      library IEEE;
88      use IEEE.std_logic_1164.all;
89
90      package body std_logic_arith is
91          -- synopsis synthesis_off
92          type tbl_type is array (STD_ULOGIC) of STD_ULOGIC;
93          constant tbl_BINARY : tbl_type :=
94              ('X', 'X', '0', '1', 'X', 'X', '0', '1', 'X');
95          -- synopsis synthesis_on
96
97      function CONV_INTEGER(ARG: UNSIGNED) return INTEGER is
98          variable result: INTEGER;
99          variable tmp: STD_ULOGIC;
100         -- synopsis built_in SYN_UNSIGNED_TO_INTEGER
101         begin
102             -- synopsis synthesis_off
103             assert ARG'length <= 31
104                 report "ARG is too large in CONV_INTEGER"
105                 severity FAILURE;
106             result := 0;
107             for i in ARG'range loop
108                 result := result * 2;

```

```
109         tmp := tbl_BINARY(ARG(i));
110         if tmp = '1' then
111             result := result + 1;
112         elsif tmp = 'X' then
113             assert false
114             report "CONV_INTEGER: There is an 'U'|'X'|'W'|'Z'|'-' in
an arithmetic operand, and it has been converted to 0."
115             severity WARNING;
116         end if;
117     end loop;
118     return result;
119     -- synopsis synthesis_on
120 end;
```