

Cosa è la Sintesi ?

- Sintesi è un termine generale che descrive il processo di trasformazione di un modello solitamente descritto in HDL, da un livello di astrazione ad uno più basso e più dettagliato.
- Queste trasformazioni sono finalizzate a raggiungere degli obiettivi di progetto (e.g., area, speed, power dissipation) soddisfacendo alcuni vincoli (e.g., I/O rates, sample period)

Livelli di sintesi

- Behavioral Synthesis: sintesi di una descrizione algoritmica di alto livello
 - Richiede “scheduling” e “assignment”
- Sintesi RTL (Register-Transfer Level) : sintesi di una descrizione definita a livello di registri
- Sintesi Logica: sintesi a partire da una descrizione in logica booleana

Livelli di sintesi

VHDL Descriptions at:

Algorithmic
Level

Combinational logic,
clocked registers, state
machines, memories


Boolean equations

Structural gate
net lists, technology
libraries


Behavioral
Synthesis

RTL
Synthesis



Logic
Synthesis

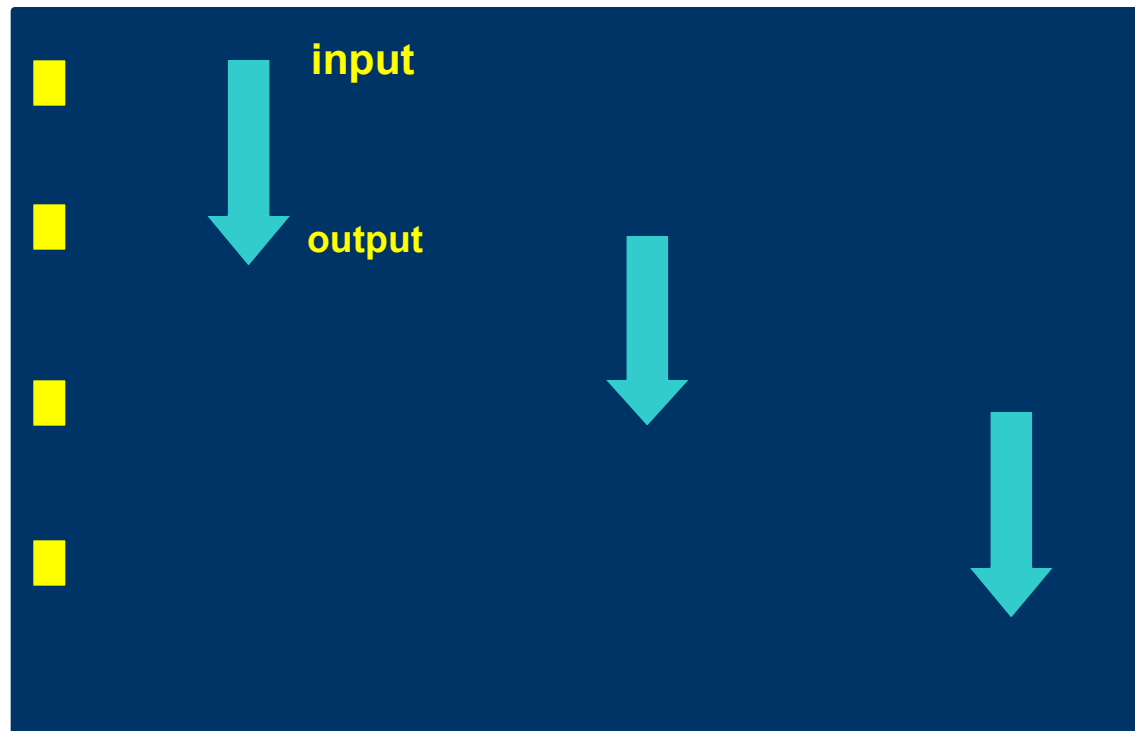



Behavioral Synthesis

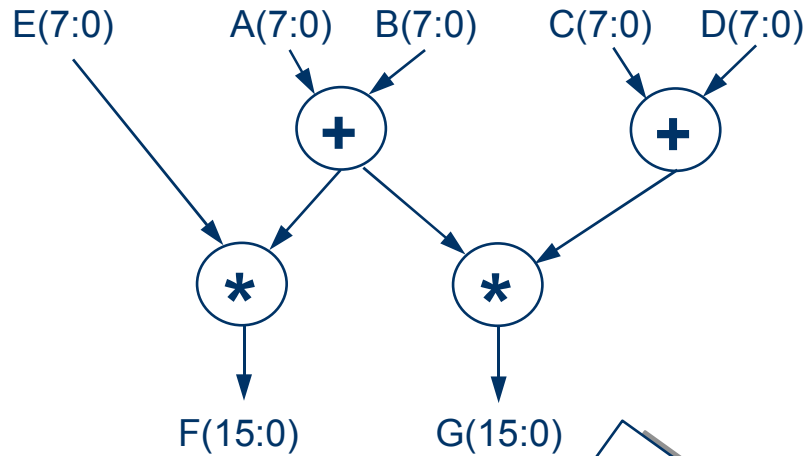

  
```
f <= (a + b) * e;  
g <= (a + b) * (c + d);
```




Behavioral Synthesis (Cont.)

  

Data Path Behavior

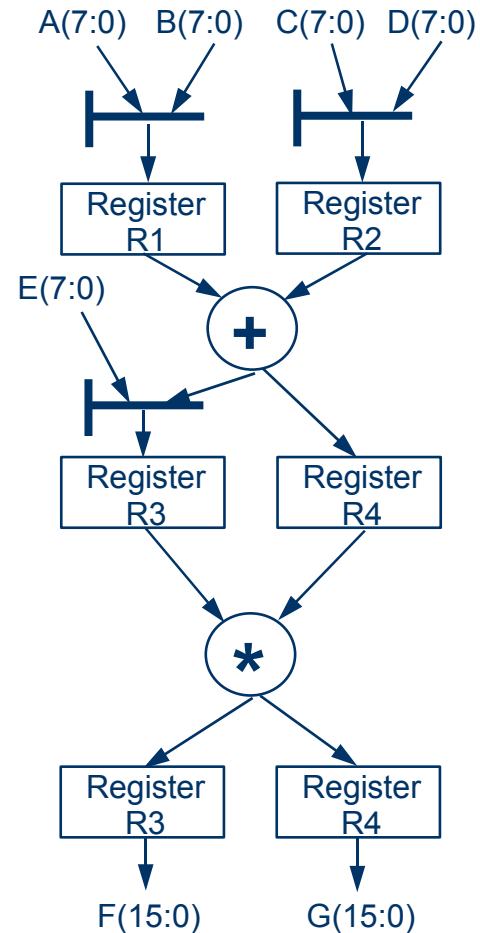


Control Flow (not all shown)

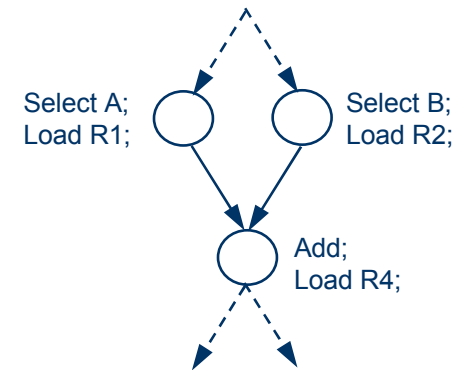


RTL Level Synthesis


Data Path Behavior

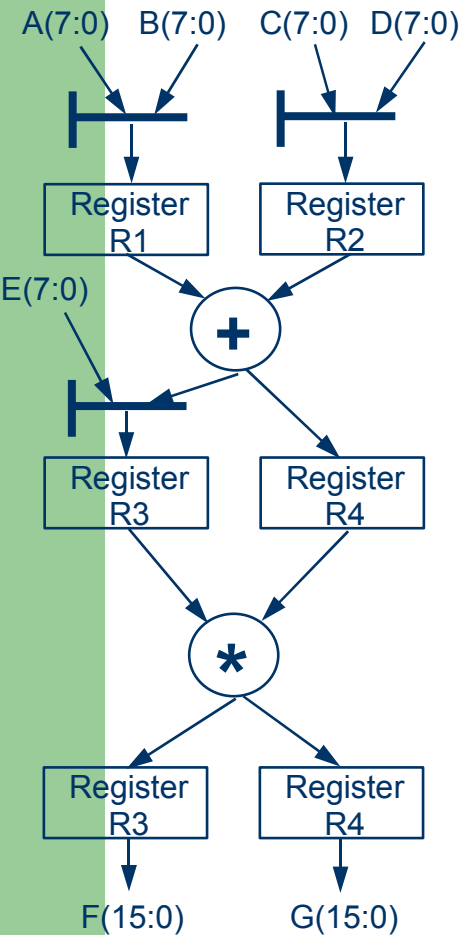


Control Flow (not all shown)

 

RTL Structure (not all shown)

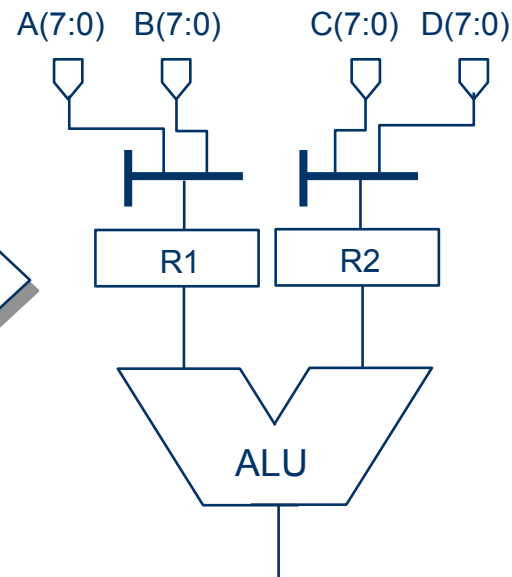


RTL Control Flow (not all shown)



 


Logic Synthesis


RTL Structure
(not all shown)

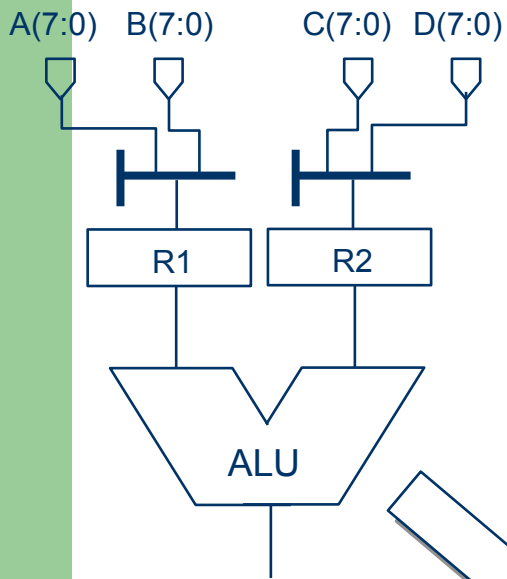

RTL Control Flow
(not all shown)

 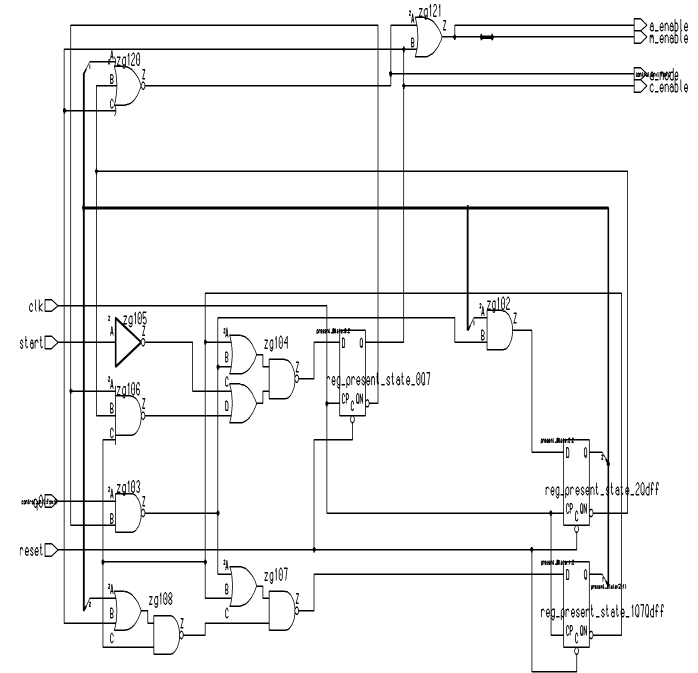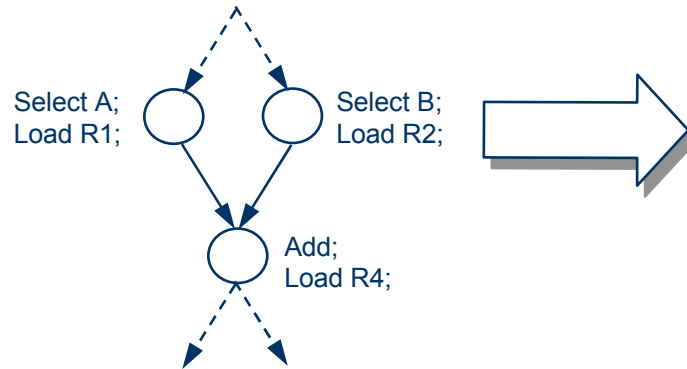

Sintesi di Loop Sequenziali

 


```
ARCHITECTURE behavior OF shift4 IS
  SIGNAL in_temp  : std_logic_vector(5
DOWNTO 0);
  SIGNAL out_temp : std_logic_vector(5
DOWNTO 1);
  BEGIN
    in_temp(0) <= shift_in;
    in_temp(4 DOWNTO 1) <= a;
    in_temp(5) <= '0';
    comb : PROCESS(mode,in_temp,a)
      BEGIN
        FOR i IN 1 TO 5 LOOP
          IF(mode = '0') THEN
            out_temp(i) <= in_temp(i-1);
          ELSE
            out_temp(i) <= in_temp(i);
          END IF;
        END LOOP;
      END PROCESS comb;
    y <= out_temp(4 DOWNTO 1);
    shift_out <= out_temp(5);
  END behavior;
```


Process Statements Example

```
ENTITY aoi_process is
  PORT(a : IN  std_logic;
        b : IN  std_logic;
        c : IN  std_logic;
        y : OUT std_logic);
END aoi_process;

 ARCHITECTURE behavior OF aoi_process IS
  SIGNAL zg1 : std_logic;
BEGIN
  comb : PROCESS(a,b,c,zg1)
  BEGIN
    zg1 <= a AND b;
    y <= not(zg1 or c);
  END PROCESS comb;
END behavior;
```




Conditional Signal Assignment

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY mux2 is
    PORT(a      : IN  std_logic;
         b      : IN  std_logic;
         sel    : IN  std_logic;
         y      : OUT std_logic);
END mux2;

ARCHITECTURE behavior OF mux2 IS

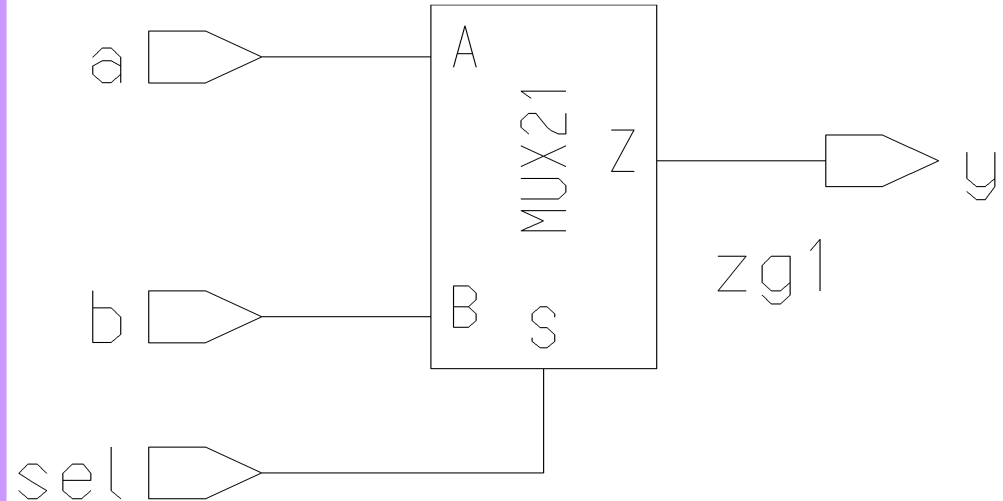
    BEGIN
        y <= a WHEN (sel = '0') ELSE
            b WHEN (sel = '1') ELSE
                'X';
    END behavior;
```



Selected Signal Assignment

```
ENTITY mux4 is
  PORT (a    : IN  std_logic;
        b    : IN  std_logic;
        c    : IN  std_logic;
        d    : IN  std_logic;
        sel  : IN  std_logic_vector(1 DOWNTO 0);
        y    : OUT std_logic);
END mux4;

 ARCHITECTURE behavior OF mux4 IS
  BEGIN
    WITH sel SELECT
      y <= a WHEN "00",
          b WHEN "01",
          c WHEN "10",
          d WHEN "11",
          'X' WHEN OTHERS;
  END behavior;
```




Procedures and Functions

```
PACKAGE BODY logic_package IS
  FUNCTION majority(in1, in2, in3 : std_logic) RETURN std_logic IS
    VARIABLE result : std_logic;
  BEGIN
    IF((in1 = '1' and in2 = '1') or (in2 = '1' and in3 = '1') or
      (in1 = '1' and in3 = '1')) THEN
      result := '1';
    ELSIF((in1 = '0' and in2 = '0') or (in2 = '0' and in3 = '0') or
      (in1 = '0' and in3 = '0')) THEN
      result := '0';
    ELSE result := 'X';
    END IF;
    RETURN result;
  END majority;
END logic_package;
```

```
USE work.logic_package.all;

ENTITY voter IS
  PORT(a : IN  std_logic;
        b : IN  std_logic;
        c : IN  std_logic;
        y : OUT std_logic);
END voter;
```
 
```
ARCHITECTURE maj OF voter IS
  BEGIN
    y <= majority(a,b,c);
  END maj;
```




Edge Sensitive D Flip-Flop

```
library IEEE;
use IEEE.std_logic_1164.all;


ENTITY d_ff IS
    PORT(d      : IN  std_logic;
         clk    : IN  std_logic;
         q      : INOUT std_logic;
         qn     : OUT std_logic);
END d_ff;

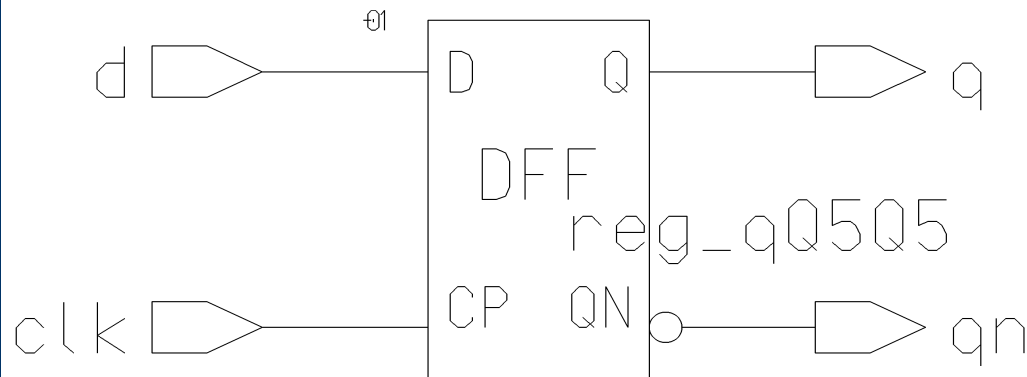ARCHITECTURE behavior OF d_ff IS
    BEGIN
        seq : PROCESS(clk)
            BEGIN
                IF(rising_edge(clk))
THEN
                    q <= d;
                END IF;
            END PROCESS seq;
            qn <= not q;
        END behavior;
```



Inferring Latches

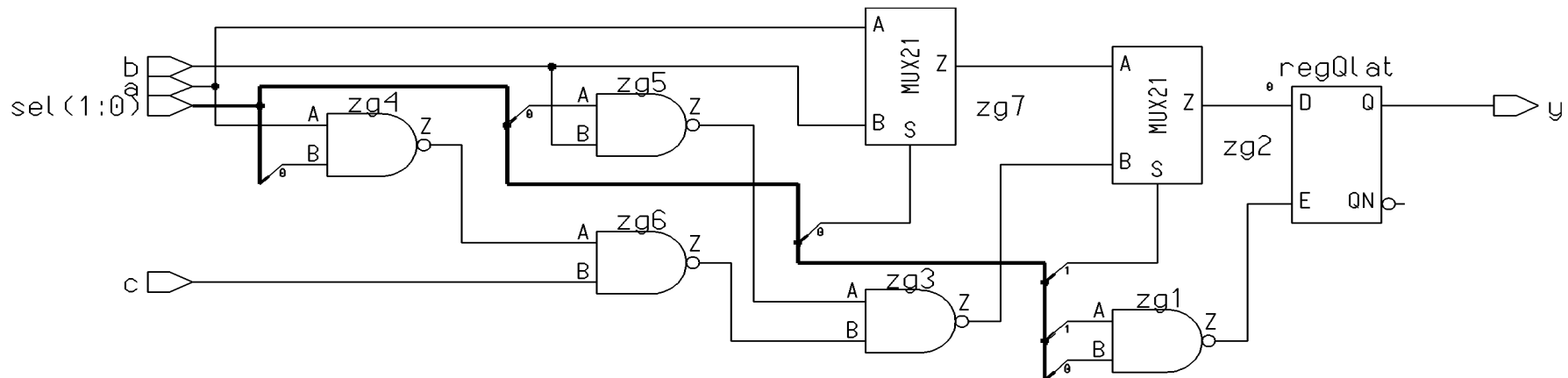
```
ARCHITECTURE behavior OF mux3_seq IS
BEGIN
  comb : PROCESS(a,b,c,sel)
  BEGIN
    CASE sel IS
      WHEN "00" => y <= a;
      WHEN "01" => y <= b;
      WHEN "10" => y <= c;
      WHEN OTHERS => --empty
    END CASE;
  END PROCESS comb;
END behavior;
```



Avoiding Latches


- Assigning values of “don’t care” (‘X’ or ‘-’) in these cases can avoid this
 
```
ARCHITECTURE behavior OF mux3 IS  
  
BEGIN  
  comb : PROCESS(a,b,c,sel)  
    BEGIN  
      CASE sel IS  
        WHEN "00" => y <= a;  
        WHEN "01" => y <= b;  
        WHEN "10" => y <= c;  
        WHEN OTHERS => y <= 'X';  
      END CASE;  
    END PROCESS comb;  
END behavior;
```




Inferring Latches in Complex Behaviors
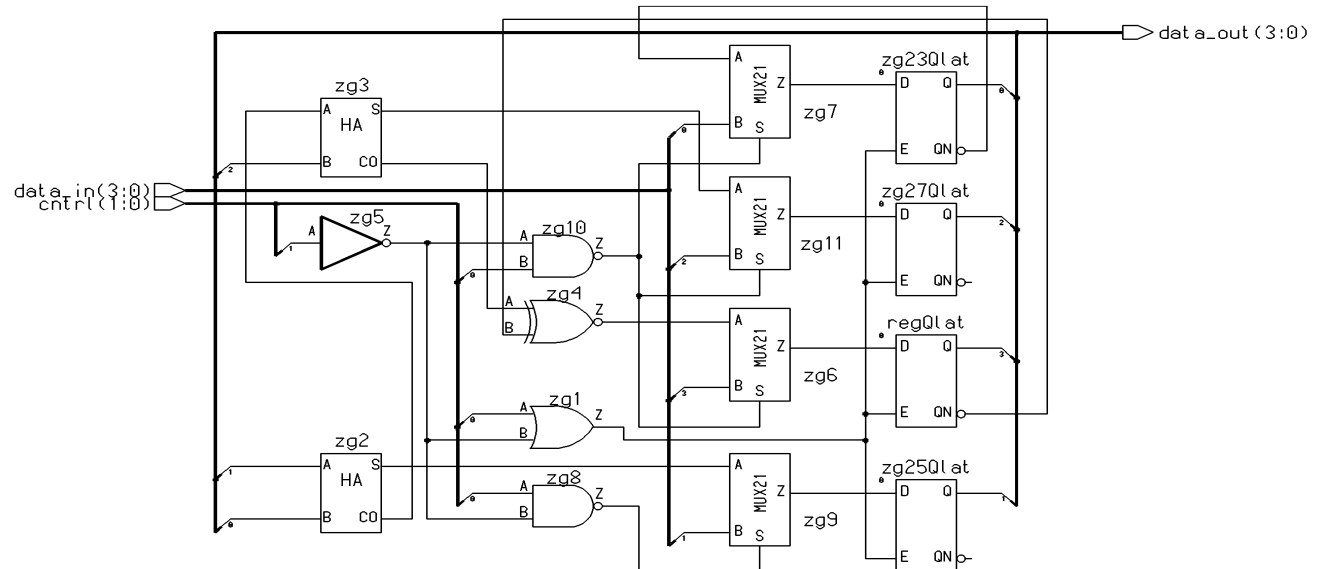
```
ARCHITECTURE rtl OF pc_comb IS
  SIGNAL pc : unsigned(3 DOWNTO 0);
  BEGIN
    one : PROCESS(data_in, cntrl, pc)
      BEGIN
        CASE cntrl IS
          WHEN "01" => pc <= (pc + "0001");
          WHEN "10" => pc <= pc;
          WHEN OTHERS => pc <= data_in;
        END CASE;
      END PROCESS one;
      DATA_OUT <= pc;
    END rtl;
```



Synchronous RTL Synthesis Example

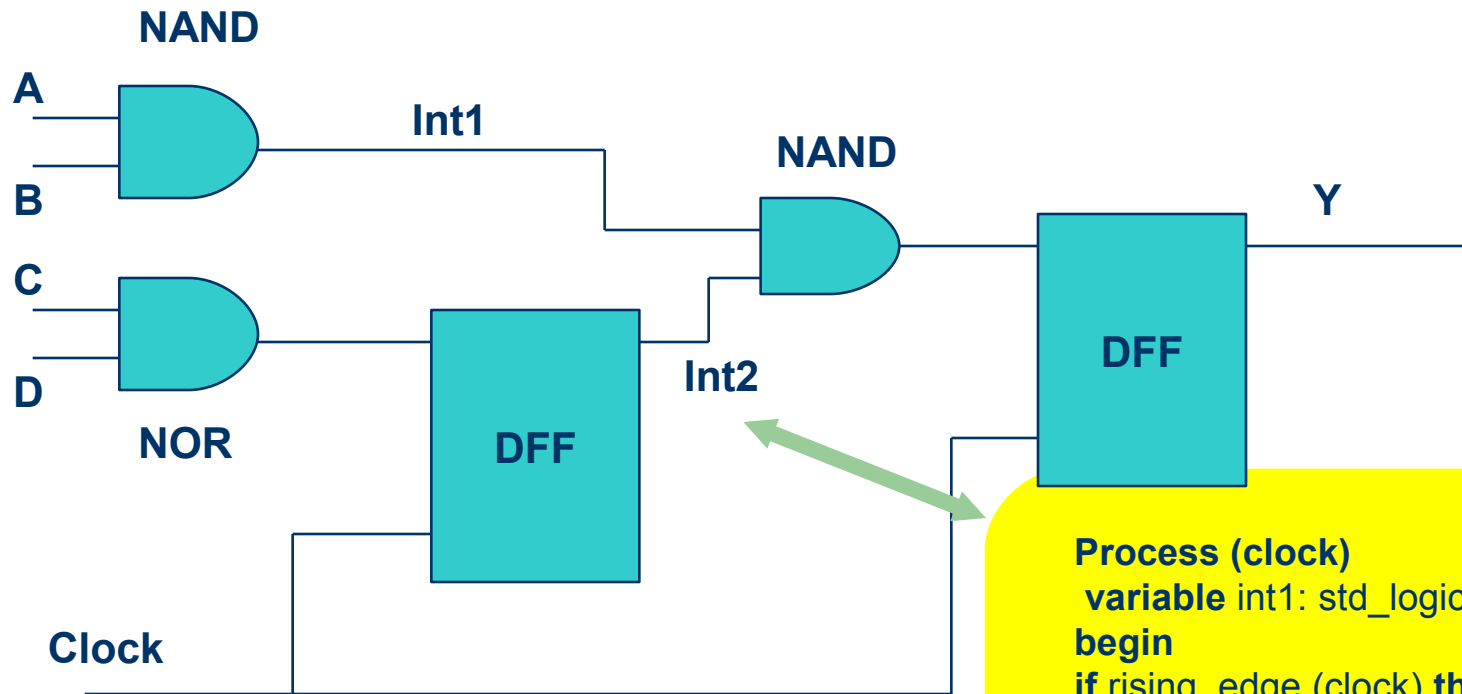

Note: **variable** int1 does not infer FF (because it is assigned to before being read, however Y and int2 infer FFs. Sensitivity list only contains the clock and asynchronous set/reset (if present). A, B, C, are not included.

```
Process (clock)
  variable int1: std_logic
begin
  if rising_edge (clock) then
    int1 := A nand B;
    int2 <= C nor D;
    Y <= int2 nand int1 ;
  end if ; end process;
```

Logic Level Optimizations

Common operations at this level include *factorization* and *flattening*, to name a few. Extensive literature on optimization at this level exists.

Original equation

$$\begin{aligned} Y &= A.B.C \\ Y2 &= Y + A.B.D \\ Y3 &= A.B + C + D \end{aligned}$$



Flatten

$$\begin{aligned} Y2 &= A.B.C + A.B.D \\ Y3 &= A.B + C + D \end{aligned}$$

Factorize



$$\begin{aligned} M &= A.B \\ Y &= M.C \\ Y2 &= Y + M.D \\ Y3 &= M + C + D \end{aligned}$$

Six gates



Factorize

$$\begin{aligned} M &= A.B, \\ N &= C + D, \quad Y2 = M.N \\ Y3 &= M + N \end{aligned}$$

Four gates